Name: Thang Nguyen
Class: ECE 486
Date: 10/2/19

As the $t \to \infty$:

The transfer function seen by v_{in}:

$$\frac{V_o(s)}{V_{in}(s)} = \frac{V_o}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

Using the result in the time domain:

$$\frac{v_o}{v_{in}} = \frac{R_2}{R_1 + R_2}$$

Using constant multiple of a linear circuit theorem:

$$\frac{v_o}{v_{in}} = \frac{v_{out}}{v_{in}} = \frac{R_2}{R_1 + R_2}$$

$$v_{out} = v_{in} \cdot \frac{R_2}{R_1 + R_2}$$

Using the v_{out} to zero for v_2 and v_3:

$$\frac{v_o}{v_{in}} = \frac{v_{out}}{v_2} = \frac{R_2}{R_1 + R_2}$$

$$v_{out} = v_2 \cdot \frac{R_2}{R_1 + R_2}$$

As the $t \to \infty$:

The open-loop function transfer (switches replaced = removed):

$$\frac{V_o(s)}{V_{in}(s)} = T_{OL}(s) = \frac{1}{1 + \frac{1}{sRC}} = \frac{sRC}{sRC + 1}$$

The system has a zero at the origin.

Open circuit the positive (switches removed):

$$V_o = \frac{R_2}{R_1 + R_2} V_{in} = \frac{0}{R_1 + R_2} = 0$$

$$V_o = 0$$

As the $t \to \infty$:

Short circuit the negative (switches removed):

$$I_{sc} = \frac{V_{in}}{R_1} = \frac{V_{in}}{R_1} = \frac{V_{in}}{R_1}$$

$$I_{sc} = \frac{V_{in}}{R_1}